



maximum length of a 7bit LFSR, tap stage 6 and 7  
 you can extend the number of stages by connecting multiple devices  
 longer sequences will can be used as noise sources  
 other taps and shorter sequences will create grainy tones and stuttering loops.